


needs to be high
For addition
* Needs to be low for
Sub

needs to be low
For Sub and odd

sub
Subtract

slt
Set on less than

beq
branch if equal

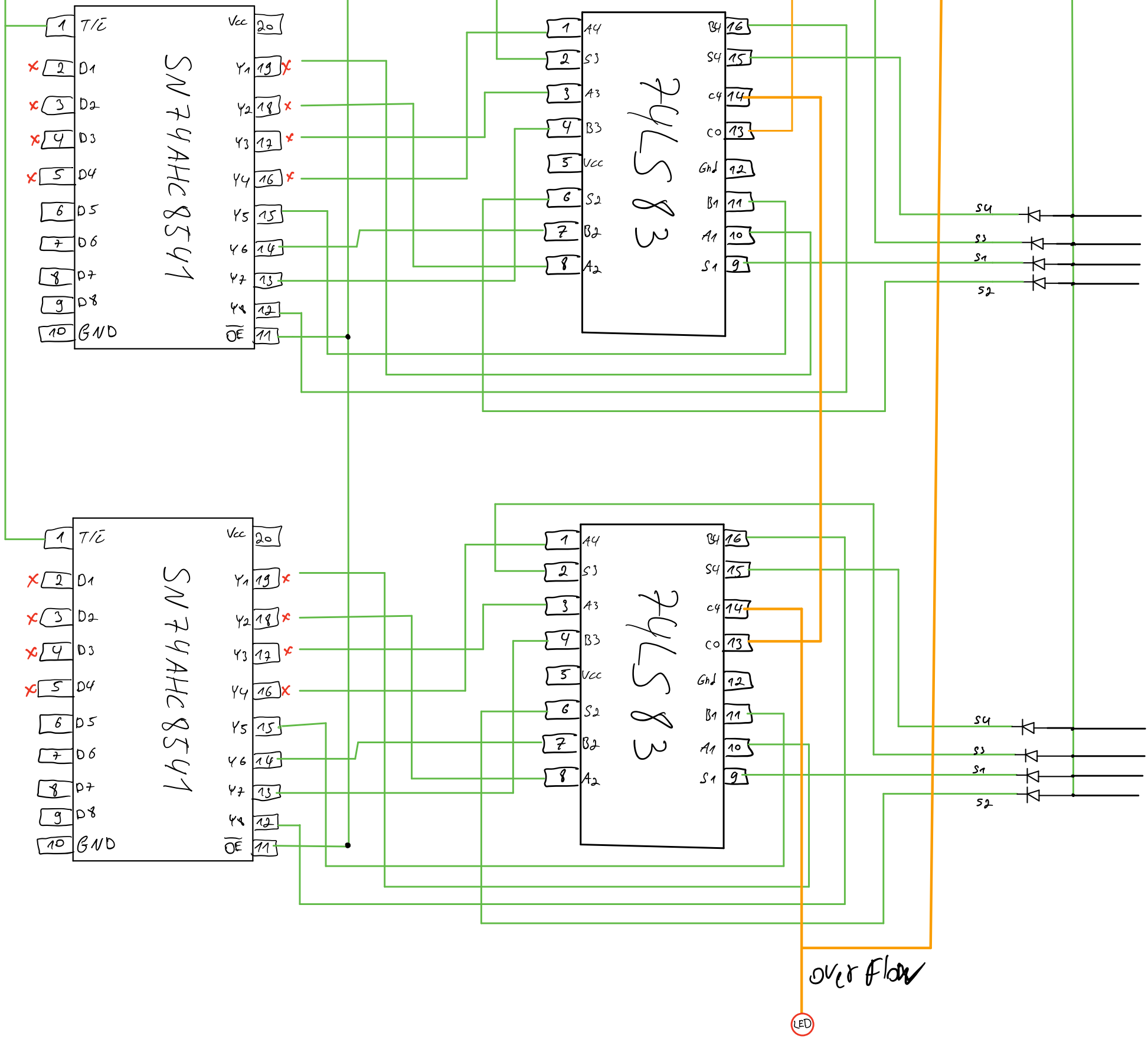

slt

The slt command will take the value of the slt line, either 0/1 and save it into a register

Diode

